

Disciplina: ELE1717 - Sistemas Digitais Curso: Engenharia Mecatrônica
--

Material de suporte - Exemplo de como implementar um circuito com apenas uma porta lógica.

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity ckt is  
    port (a,b: in std_logic;  
          x: out std_logic);  
end ckt;  
  
architecture log of ckt is  
  
begin  
    x <= a or b;  
end log;
```

Disciplina: ELE1717 - Sistemas Digitais Curso: Engenharia Mecatrônica
--

Material de suporte - Exemplo de circuito com múltiplas portas lógicas encadeadas.

```
library ieee;
use ieee.std_logic_1164.all;

entity ckt is
    port (a,b,c: in std_logic;
          x: out std_logic);
end ckt;

architecture log of ckt is

    signal aux1 : std_logic;
    signal aux2 : std_logic;
    signal aux3 : std_logic;

begin
    aux1 <= b and c;
    aux2 <= a and c;
    aux3 <= a and b;
    x <= aux1 or aux2 or aux3;
end log;
```

Disciplina: ELE1717 - Sistemas Digitais Curso: Engenharia Mecatrônica
--

Material de suporte - Exemplo de circuito com múltiplas portas lógicas em linha.

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity ckt is  
    port (a,b,c: in std_logic;  
          x: out std_logic);  
end ckt;  
  
architecture log of ckt is  
  
begin  
    x <= (b and c) or (a and c) or (a and b);  
end log;
```

Disciplina: ELE1717 - Sistemas Digitais Curso: Engenharia Mecatrônica
--

Material de suporte - Vetores

```
library ieee;
use ieee.std_logic_1164.all;

entity ckt is
    port (a,b: in  std_logic_vector(0 to 3);
          x: out std_logic_vector(0 to 3));
end ckt;

architecture log of ckt is

begin
    x <= a and b;
end log;
```

Material de suporte - Vetores

```
library ieee;
use ieee.std_logic_1164.all;

entity ckt is
    port (a,b: in  std_logic_vector(0 to 3);
          x: out std_logic_vector(0 to 3));
end ckt;

architecture log of ckt is

begin
    x(3) <= a(3) and b(3);
    x(2) <= a(2) and b(2);
    x(1) <= a(1) and b(1);
    x(0) <= a(0) and b(0);
end log;
```

Disciplina: ELE1717 - Sistemas Digitais Curso: Engenharia Mecatrônica
--

Material de suporte - Componentes

```
library ieee;
use ieee.std_logic_1164.all;

entity C1 is
    port (x,y: in  std_logic;
          z: out std_logic);
end C1;

architecture log of C1 is

begin
    z <= x or y;
end log;

entity C2 is
    port (x: in  std_logic;
          z: out std_logic);
end C2;

architecture log of C2 is

begin
    z <= not x;
end log;

entity ckt is
    port (a,b: in  std_logic;
          w: out std_logic);
end ckt;

architecture log of ckt is

component C1 is
    port (x,y: in  std_logic;
          z: out std_logic);
end component;

component C2 is
    port (x: in  std_logic;
          z: out std_logic);
end component;

signal s: std_logic;
begin
    U1: C1 port map(a,b,s);
    U2: C2 port map(s,w);
end log;
```

Disciplina: ELE1717 - Sistemas Digitais Curso: Engenharia Mecatrônica
--

Material de suporte - Componentes

```
library ieee;
use ieee.std_logic_1164.all;

entity C_ONES is
    port (a,b,c: in std_logic;
          x: out std_logic);
end C_ONES;

architecture log of C_ONES is

begin
    x <= (b and c) or (a and c) or (a and b);
end log;

entity ckt is
    port (a,b: in std_logic_vector(2 downto 0);
          w: out std_logic);
end ckt;


architecture log of ckt is

component C_ONES is
    port (a,b,c: in std_logic; x:out std_logic);
end component;

signal s1,s2: std_logic;
begin
    U1: C_ONES port map(a(2),a(1),a(0),s1);
    U2: C_ONES port map(b(2),b(1),b(0),s2);
    w <= s1 or s2;
end log;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - Flip-Flop D

 


```
library ieee;
use ieee.std_logic_1164.all;

entity ffd is
    port (ck, clr, set, d : in  std_logic;
          q : out std_logic);
end ffd;

architecture logica of ffd is
begin
    process(ck, clr, set)
    begin
        if      (set = '0')           then q <= '1';
        elsif  (clr = '0')           then q <= '0';
        elsif  (ck'event and ck = '1') then q <= d;
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - Registrador de 3 bits com entradas síncronas




```
library ieee;
use ieee.std_logic_1164.all;

entity reg3bs is
    port (ck, clr, set : in  std_logic;
          d : in  std_logic_vector(2 downto 0);
          q : out std_logic_vector(2 downto 0));
end reg3bs;

architecture logica of reg3bs is
begin
    process (ck)
    begin
        if (ck'event and ck = '1') then
            if (clr = '1') then q <= "000"; -- condicao do sinal relógio
            elsif (set = '1') then q <= "111"; -- teste para levar q=000
            else q <= d; -- teste para levar q=111
            end if;
        end if;
    end process;
end logica;
```


Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - Registrador de 3 bits com entradas assíncronas




```
library ieee;
use ieee.std_logic_1164.all;

entity reg3ba is
    port (ck, clr, set : in  std_logic;
          d : in  std_logic_vector(2 downto 0);
          q : out std_logic_vector(2 downto 0));
end reg3ba;

architecture logica of reg3ba is
begin
    process (ck, clr, set)
    begin
        if      (clr = '1')           then q <="000"; -- q=000 independente de ck
        elsif  (set = '1')           then q <="111"; -- q=111 independente de ck
        elsif  (ck'event and ck = '1') then q <=d;    -- condicao do sinal relógio
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - Registrador de 3 bits com entradas assíncronas e habilitador




```
library ieee;
use ieee.std_logic_1164.all;

entity reg3ba_en is
    port (ck, clr, set, ld : in  std_logic;
          d : in  std_logic_vector(2 downto 0);
          q : out std_logic_vector(2 downto 0));
end reg3ba_en;

architecture logica of reg3ba_en is
begin
    process (ck, clr, set)
    begin
        if (clr = '1') then q <= "000";    -- q=000 independente de ck
        elsif (set = '1') then q <= "111"; -- q=111 independente de ck
        elsif (ck'event and ck = '1') then -- detecta borda de ck
            if (ld = '1') then q <= d;     -- verifica habilitacao
            end if;
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - MDE sequencial

 

```


use ieee.std_logic_1164.all;

entity mde is
  port (ck, rst : in std_logic;
        q       : out std_logic_vector(1 downto 0));
end mde;

architecture logica of mde is
begin
  process (ck, rst)
  begin
    if rst = '1' then
      q <= "00";
    elsif (ck'event and ck = '1') then
      case q is
        when "00" => q <= "01";
        when "01" => q <= "11";
        when "11" => q <= "10";
        when "10" => q <= "00";
      end case;
    end if;
  end process;
end logica;
  
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - MDE do tipo Moore com um processo



```
use ieee.std_logic_1164.all;

entity mde is
    port (ck, rst, s : in std_logic;
          q : out std_logic_vector(1 downto 0));
end mde;


architecture logica of mde is
    type st is (A, B, C, D);
    signal estado : st;

begin
    process (ck, rst)
    begin
        if rst = '1' then
            estado <= A;
        elsif (ck'event and ck = '1') then
            case estado is
                when A =>
                    if s = '1' then estado <= B;
                    else estado <= D;
                    end if;
                when B =>
                    if s = '1' then estado <= C;
                    else estado <= A;
                    end if;
                when C =>
                    if s = '1' then estado <= D;
                    else estado <= B;
                    end if;
                when D =>
                    if s = '1' then estado <= A;
                    else estado <= C;
                    end if;
            end case;
        end if;
    end process;

    with estado select
        q <= "00" when A,
             "01" when B,
             "11" when C,
             "10" when D;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - MDE do tipo Moore com dois processos



```

library ieee;
use ieee.std_logic_1164.all;

entity mde_b is
    port (ck, rst, w : in std_logic;
          z : out std_logic);
end mde_b;

architecture logica of mde_b is
    type state_type is (a, b, c);
    signal y_present, y_next : state_type;


begin
    process (w, y_present)
    begin
        case y_present is
            when a =>
                if w = '0' then y_next <= a;
                else y_next <= b; end if;
            when b =>
                if w = '0' then y_next <= a;
                else y_next <= c; end if;
            when c =>
                if w = '0' then y_next <= a;
                else y_next <= c; end if;
        end case;
    end process;

    process (ck, rst)
    begin
        if rst = '0' then
            y_present <= a;
        elsif (ck'event and ck = '1') then
            y_present <= y_next;
        end if;
    end process;

    z <= '1' when y_present = c else '0';
end logica;
  
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - MDE do tipo Mealy

 

```

library ieee;
use ieee.std_logic_1164.all;

entity mde_d is
    port (ck, rst, w : in std_logic;
          z : out std_logic);
end mde_d;


architecture logica of mde_d is
    type state_type is (a, b);
    signal y : state_type;

begin
    process (rst, ck)
    begin
        if rst = '0' then
            y <= a;
        elsif (ck'event and ck = '1') then
            case y is
                when a =>
                    if w = '0' then y<=a;
                    else y<=b; end if;
                when b =>
                    if w = '0' then y<=a;
                    else y<=b; end if;
            end case;
        end if;
    end process;

    process (y, w)
    begin
        case y is
            when a => z <= '0';
            when b => z <= w;
        end case;
    end process;
end logica;
  
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - Memória ROM

 

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity s_rom is
    port (clk : in std_logic;
          en  : in std_logic;
          addr: in std_logic_vector( 1 downto 0);
          data: out std_logic_vector(11 downto 0));
end s_rom;

architecture logica of s_rom is

    type rom is array (0 to 3) of std_logic_vector(11 downto 0);
    signal memoria : rom := (x"401",x"411",x"412",x"413");
    signal r_addr   : std_logic_vector(0 to 1);

begin
    process(clk)
    begin
        if rising_edge(clk) then
            if en='1' then
                r_addr <= addr;
            end if;
        end if;
    end process;
    data <= memoria(to_integer(unsigned(r_addr)));
end logica;
```